




# Loop Analysis (Mesh Analysis) (DC Excitation)

Note: procedure to solve problems on loop analysis (Both DC & AC excitations)

- i) Identify the number of meshes
- ii) Assign clockwise direction for mesh currents
- iii) To identify essential, nonessential and supermesh; in place of current source put a open and the remaining elements as lines.

 This is a essential mesh and we write KVL equation (for closed path)

 This is a nonessential mesh and we write KCL equation (for current source)

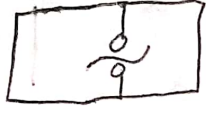 This is supermesh and we write KVL & KCL equations.  
Two conditions has to be met to form a super mesh


- i) Meshes has to merge
- ii) The outer path should be a closed path.

(only when there is a current source in a circuit, we come across nonessential & supermesh)

- iv) Equations are sorted out & by making use of calculator, solve the simultaneous equations for unknown currents  $I_1, I_2, \dots$
- v) Voltage across elements & power dissipated can be obtained by using mesh currents.

Prob: Write the mesh equations for the circuit shown in figure and determine mesh currents using mesh analysis.

Sol:

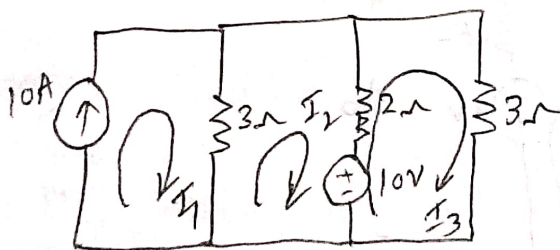

Rough Work (procedure iii)

0	NE	FM	EM
9			

KCL equation for non-essential mesh 1 :  $I_1 = +10$

KVL equation for essential mesh 2 :  $3(I_2 - I_1) + 2(I_2 - I_3) + 10 = 0$

KVL equation for essential mesh 3 :  $-10 + 2(I_3 - I_2) + 3I_3 = 0$

Sorting the above equations: (1)  $I_1 + (0)I_2 + (0)I_3 = 10$



$$(-3)I_1 + (5)I_2 + (-2)I_3 = -10$$

$$(0)I_1 + (-2)I_2 + (5)I_3 = 10$$

Using calculator,  $I_1 = 10A$ ,  $I_2 = 5.714A$ ,  $I_3 = 4.285A$

Prob: For the circuit shown in the figure, solve for mesh currents.

Sol:

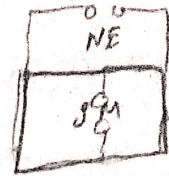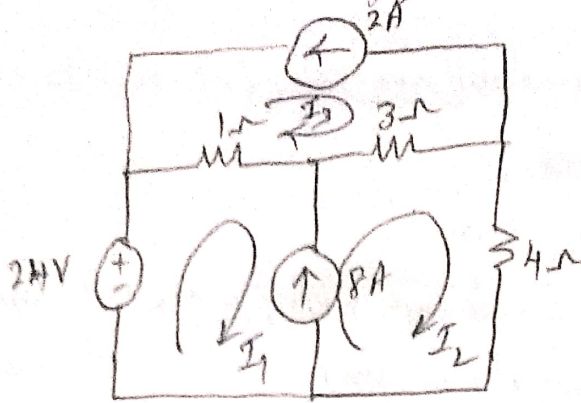

outer path of SM is closed path (To apply KVL)

KCL equation to nonessential mesh 3:  $I_3 = -2$

KCL equation to supermesh 1 & 2:  $I_2 - I_1 = 8$

KVL equation to supermesh 1 & 2:  $-24 + 1(I_1 - I_3) + 3(I_2 - I_3) + 4I_2 = 0$

$$(0)I_1 + (0)I_2 + (1)I_3 = -2$$

$$(-1)I_1 + (1)I_2 + (0)I_3 = 8$$

$$(1)I_1 + (7)I_2 + (-4)I_3 = 24$$



$$I_1 = -5A$$

$$I_2 = 3A$$

$$I_3 = -2A$$

Prob: Find  $V_o$  in the circuit shown in the figure using mesh analysis.

Sol:

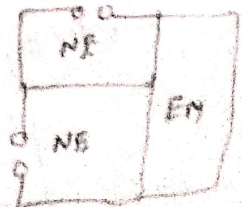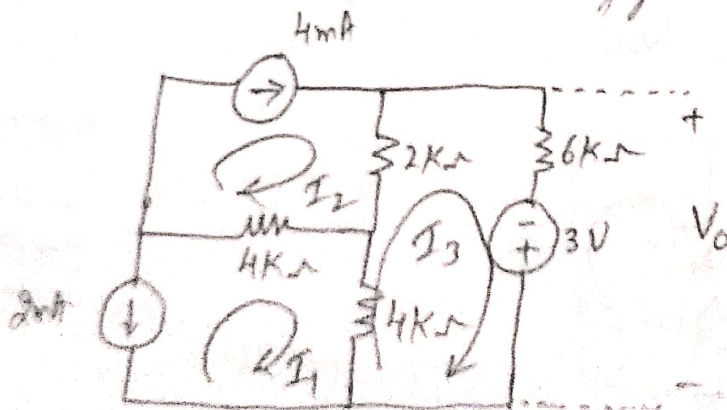

KCL equation for non-essential mesh 1:  $I_1 = -2 \times 10^{-3}$

KCL equation for non-essential mesh 2:  $I_2 = +4 \times 10^{-3}$

KVL equation for essential mesh 3:  $4K(I_3 - I_1) + 2K(I_3 - I_2) + 6K I_3 - 3 = 0$

$$(1) I_1 + (0) I_2 + (0) I_3 = -2 \times 10^{-3}$$

$$(0) I_1 + (1) I_2 + (0) I_3 = 4 \times 10^{-3}$$

$$(-4K) I_1 + (-2K) I_2 + (12K) I_3 = 3$$


While using calculator  
in place of K use  $10^3$   
say  $-4K$  as  $-4 \times 10^3$

$$I_1 = -2 \text{ mA}$$

$$I_2 = 4 \text{ mA}$$

$$I_3 = 2.5 \times 10^{-4} \text{ A} = 0.25 \text{ mA}$$



To find  $V_0$ :

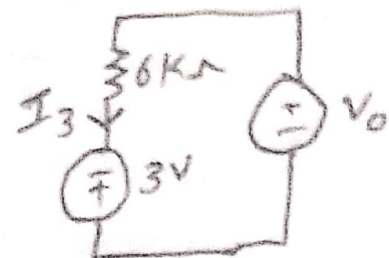

$$\begin{aligned} \text{KVL: } +3 - 6K I_3 + V_0 &= 0 \\ V_0 &= 6K I_3 - 3 \\ V_0 &= 6 \times 10^3 \times 0.25 \times 10^{-3} - 3 = 1.5 - 3 = -1.5 \text{ V} \end{aligned}$$

Q.3: For the network shown in figure find the mesh currents  $I_1$ ,  $I_2$  &  $I_3$ .

Sol:

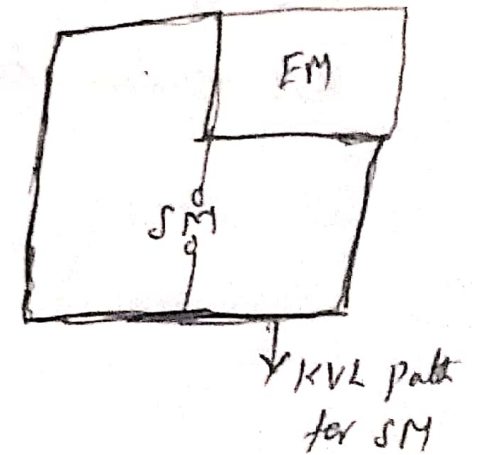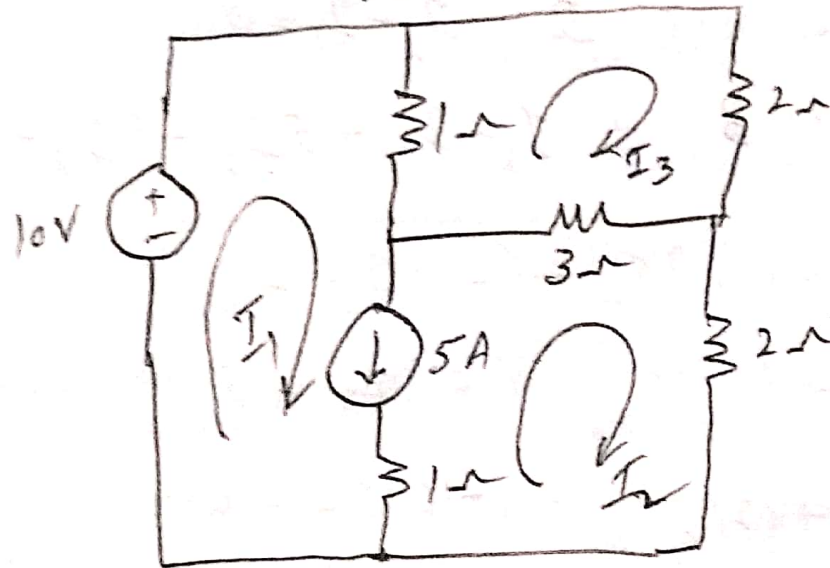

KCL equation for supermesh 1 & 2 :  $I_1 - I_2 = 5$

KVL equation for essential mesh 3 :  $1(I_3 - I_1) + 2I_3 + 3(I_3 - I_2) = 0$

KVL equation for super mesh 1 & 2 :  $-10 + 1(I_1 - I_3) + 3(I_2 - I_3) + 2I_2 = 0$

$$(1)I_1 + (-1)I_2 + (0)I_3 = 5$$

$$(-1)I_1 + (-3)I_2 + (6)I_3 = 0$$

$$(1)I_1 + (5)I_2 + (-4)I_3 = 10$$



$$I_1 = 7.5A$$

$$I_2 = 2.5A$$

$$I_3 = 2.5A$$

Prob: Determine the currents  $i_1$ ,  $i_2$  and  $i_3$  in the circuit shown in the figure using mesh current method.

Sol:

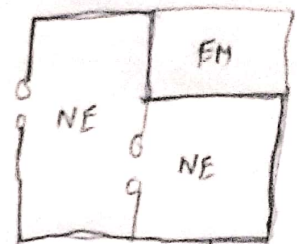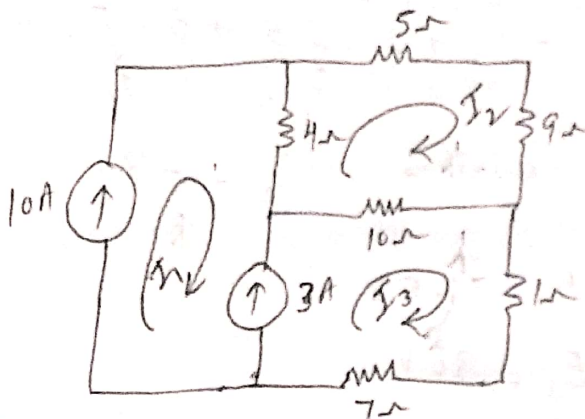

Not a supermesh,  
no closed path  
even though the meshes  
are merging (10)

KCL equation to non-essential mesh 1:  $I_1 = 10$

KCL equation to non-essential mesh 3:  $I_2 - I_1 = 3$

KVL equation to essential mesh 2:  $4(I_2 - I_1) + 5I_2 + 9I_2 + 10(I_2 - I_3) = 0$

$$(1)I_1 + (0)I_2 + (0)I_3 = 10$$

$$(-1)I_1 + (1)I_2 + (0)I_3 = 3$$

$$(-4)I_1 + (28)I_2 + (-10)I_3 = 0$$



$$I_1 = 10A$$

$$I_2 = 13A$$

$$I_3 = 32.4A$$

Prob: Determine the currents  $I_1$ ,  $I_2$  &  $I_3$  in the circuit shown in the figure using mesh current method.

Sol:

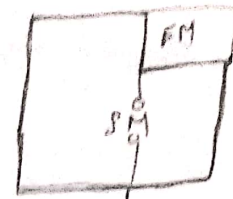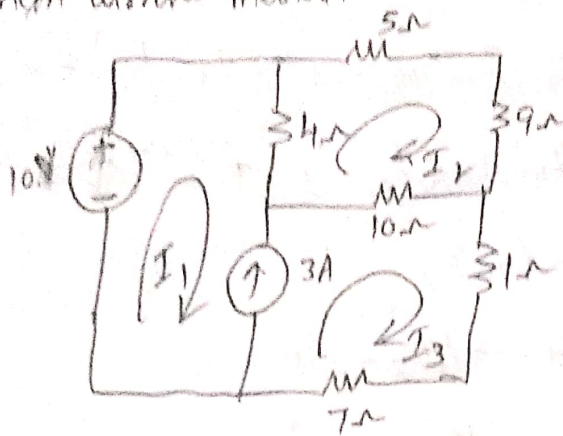

closed path to apply KVL

KCL equation to supermesh 1 & 3:  $I_3 - I_1 = 3$

KVL equation to Supermesh 1 & 3:  $-10 + 4(I_1 - I_2) + 10(I_3 - I_2) + 1I_3 + 7I_3 = 0$

KVL equation to essential mesh 2:  $4(I_2 - I_1) + 5I_2 + 9I_2 + 10(I_2 - I_3) = 0$

$$(-1)I_1 + (0)I_2 + (1)I_3 = 3$$

$$(4)I_1 + (-14)I_2 + (18)I_3 = 10$$

$$(-4)I_1 + (28)I_2 + (-10)I_3 = 0$$



$$I_1 = -1.933 \text{ A}$$

$$I_2 = 0.104 \text{ A}$$

$$I_3 = 1.066 \text{ A}$$

Prob: Using mesh current analysis determine  $V_x$  and power supplied by 10V source of the network shown in figure.

Sol:

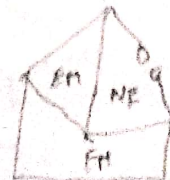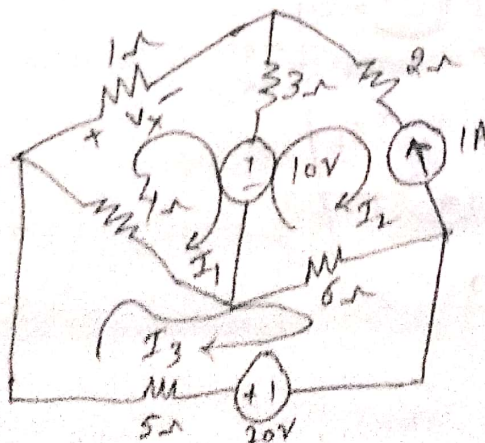

KCL to non essential mesh 2 :  $I_2 = -1$

KVL to essential mesh 1 :  $1I_1 + 3(I_1 - I_2) + 10 + 4(I_1 - I_3) = 0$

KVL to essential mesh 3 :  $4(I_3 - I_1) + 6(I_3 - I_2) - 20 + 5I_3 = 0$

$$(0)I_1 + (1)I_2 + (0)I_3 = -1$$

$$(8)I_1 + (-3)I_2 + (-4)I_3 = -10$$

$$(-4)I_1 + (-6)I_2 + (15)I_3 = 20$$

$$I_1 = -1.336 \text{ A}$$

$$I_2 = -1 \text{ A}$$

$$I_3 = 0.576 \text{ A}$$

$$V_X = +1I_1 = 1 \times -1.336 = -1.336 \text{ V}$$

$$P_{\text{absorbed}(10\text{V})} = +VI$$



$$= +(V)(I_1 - I_2)$$

$$= +(10)(-1.336 + 1)$$

$$= -3.36 \text{ W}$$

$$P_{\text{delivered}(10\text{V})} = +3.36 \text{ W}$$

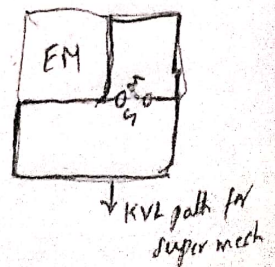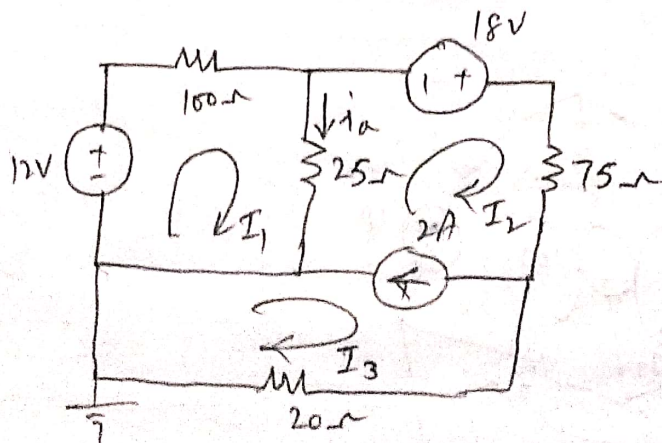Prob: Find the current  $i_a$  in the circuit shown in figure using mesh analysis.



Note: If any of the current is given as anticlockwise, make it clockwise while solving the problem. Write the current of opposite sign in the answer.

KCL to Supermesh 2 & 3:  $I_2 - I_3 = 2$

KVL to super mesh 2 & 3:  $25(I_2 - I_1) - 18 + 75I_2 + 20I_3 = 0$

KVL to essential mesh 1:  $-12 + 100I_1 + 25(I_1 - I_2) = 0$

$$(0)I_1 + (1)I_2 + (-1)I_3 = 2$$

$$(-25)I_1 + (100)I_2 + (20)I_3 = 18$$

$$(125)I_1 + (-25)I_2 + (0)I_3 = 12$$

$$I_1 = 0.20 A$$



$$I_2 = 0.52 A$$

$$I_3 = -1.47 A$$

$$I_a = I_1 - I_2 = 0.20 - 0.52 = -0.32 A$$

Prob: Find the Current in the  $24\Omega$  resistance using mesh analysis for the circuit shown in figure.

Sol:

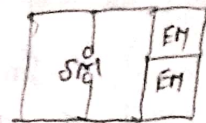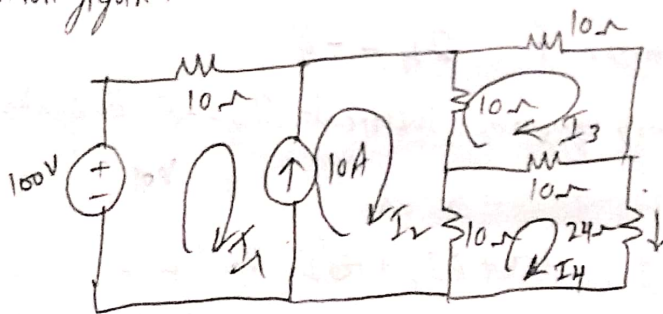

KCL equation for supermesh 1 & 2:  $I_2 - I_1 = 10 \Rightarrow I_2 = 10 + I_1$

Since we get four equations, make it as three equations by substituting  $I_2 = 10 + I_1$  in the equations below such that the unknowns will be  $I_1, I_3$  &  $I_4$

KVL equation for super mesh 1 & 2:  $-100 + 10I_1 + 10(I_2 - I_3) + 10(I_2 - I_4) = 0$

$$-100 + 10I_1 + 100 + 10I_1 - 10I_3 + 100 + 10I_1 - 10I_4 = 0$$

$$(30)I_1 + (-10)I_3 + (-10)I_4 = -100 \quad \text{--- (1)}$$

KVL equation for essential mesh 3:  $10(I_3 - (10 + I_1)) + 10I_3 + 10(I_3 - I_4) = 0$

$$10I_3 - 100 - 10I_1 + 10I_3 + 10I_3 - 10I_4 = 0$$

$$(-10)I_1 + (30)I_3 + (-10)I_4 = 100 \quad \text{--- (2)}$$

KVL equation for essential mesh 4:  $10 \times \left\{ I_4 - \underset{\substack{\leftarrow \\ I_2}}{10 + I_1}} \right\} + 10(I_4 - I_3) + 24I_4 = 0$

$$10I_4 - 100 - 10I_1 + 10I_4 - 10I_3 + 24I_4 = 0$$

$$(-10)I_1 + (-10)I_3 + (44)I_4 = 100 \quad \text{--- (3)}$$

Solving ①, ② & ③



$$X = I_1 = -1.029 \text{ A}$$

$$Y = I_3 = 3.970 \text{ A}$$

$$Z = I_4 = 2.941 \text{ A (current flowing through } 24\Omega \text{)}$$

$$I_2 = 10 + I_1 = 10 - 1.029 = 8.971 \text{ A}$$

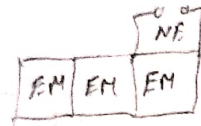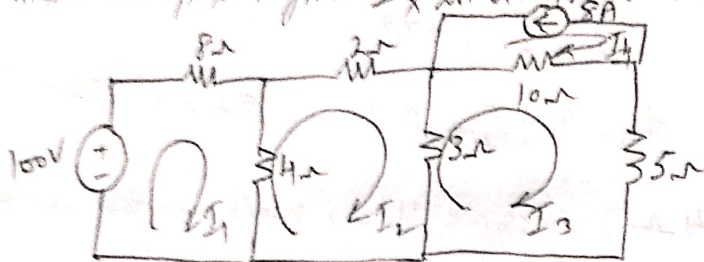Prob: Use mesh analysis to find  $I_x$  in the circuit shown in the figure.



Sol:

KCL to non-essential mesh 4:  $I_4 = -8$

In the remaining equations substitute  $I_4 = -8$ , the unknowns will be  $I_1, I_2, I_3$ .

KVL to essential mesh 1:  $-100 + 8I_1 + 4(I_1 - I_2) = 0$

$$(12)I_1 + (-4)I_2 + (0)I_3 = 100 \quad \text{--- (1)}$$

KVL to essential mesh 2:  $4(I_2 - I_1) + 2I_2 + 3(I_2 - I_3) = 0$

$$(-4)I_1 + (9)I_2 + (-3)I_3 = 0 \quad \text{--- (2)}$$

KVL to essential mesh 3:  $3(I_3 - I_2) + 10\left\{ I_3 - \underset{\substack{\leftarrow \\ I_4}}{-8} \right\} + 5I_3 = 0$

$$3I_3 - 3I_2 + 10I_3 + 80 + 5I_3 = 0$$

$$(0)I_1 + (-3)I_2 + (18)I_3 = -80 \quad \text{--- (3)}$$

Solving ①, ② & ③



$$I_1 = 9.26 \text{ A}$$

$$I_2 = 2.79 \text{ A}$$

$$I_3 = -3.97 \text{ A}$$

$$I_4 = -8 \text{ A}$$

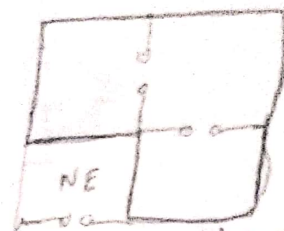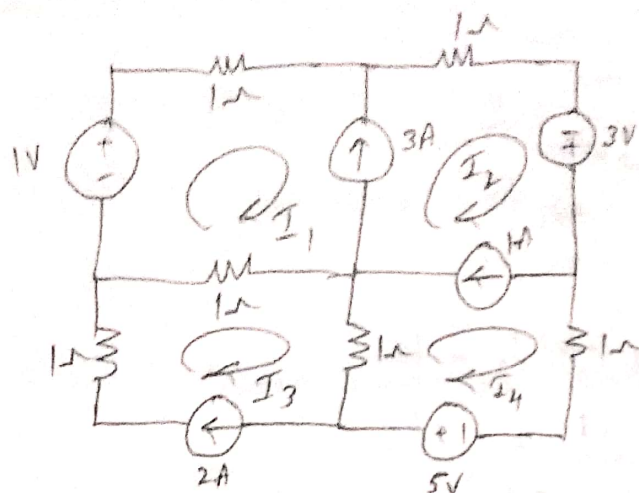Prob: Find  $I_1, I_2, I_3, I_4$  using mesh analysis



↓ KVL for super mesh 1, 2, 4

KCL equation for non-essential mesh 3:  $I_3 = 2$

In the remaining equations substitute  $I_3 = 2$ , the unknowns will be  $I_1, I_2, I_4$

KCL equation for supermesh 1, 2, 4:  $I_2 - I_1 = 3$

KCL equation for supermesh 1, 2, 4:  $I_2 - I_4 = 1$

KVL equation for supermesh 1, 2, 4:  $-1 + 1I_1 + 1I_2 - 3 + 1I_4 - 5 + 1(I_4 - 2) + 1(I_1 - 2) = 0$

$$(-1)I_1 + (1)I_2 + (0)I_4 = 3$$

$$(0)I_1 + (1)I_2 + (-1)I_4 = 1$$

$$(2)I_1 + (1)I_2 + (2)I_4 = 13$$

$$\begin{array}{r} -1 \\ -3 \\ -5 \\ -2 \\ -2 \\ \hline = 13 \text{ (RHS)} \end{array}$$

$$x = I_1 = 1.2 \text{ A}$$

$$y = I_2 = 4.2 \text{ A} \quad I_2 = 2 \text{ A}$$

$$z = I_4 = 3.2 \text{ A}$$

### Inspection method

When all the meshes are essential meshes (i.e. circuit with no current sources)

We can apply inspection method, based on  $[R][I] = [V]$

For a 3 loop problem

$$\begin{bmatrix} R_{11} & R_{12} & R_{13} \\ R_{21} & R_{22} & R_{23} \\ R_{31} & R_{32} & R_{33} \end{bmatrix} \begin{bmatrix} I_1 \\ I_2 \\ I_3 \end{bmatrix} = \begin{bmatrix} V_1 \\ V_2 \\ V_3 \end{bmatrix}$$

$V_1 \rightarrow$  first loop voltage

$V_2 \rightarrow$  second loop voltage

$V_3 \rightarrow$  third loop voltage

$R_{11} \rightarrow$  Total resistance in loop 1


$R_{22} \rightarrow$  Total resistance in loop 2

$R_{33} \rightarrow$  Total resistance in loop 3

$$\begin{aligned} R_{12} &= R_{21} = -(\text{resistance common to loop 1 \& 2}) \\ R_{13} &= R_{31} = -(\text{resistance common to loop 1 \& 3}) \\ R_{23} &= R_{32} = -(\text{resistance common to loop 2 \& 3}) \end{aligned}$$

Prob: Solve for mesh currents for the circuit shown in figure.

Sol:

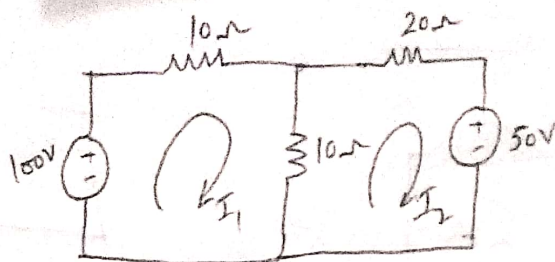


By inspection,  $(20)I_1 + (-10)I_2 = 100$

$$(-10)I_1 + (30)I_2 = -50$$

$$I_1 = 5A$$

$$I_2 = 0A$$

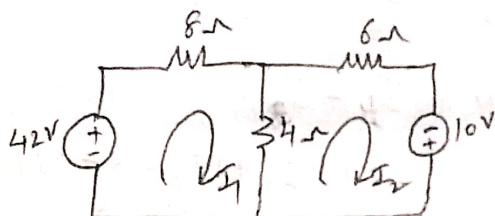Prob: Solve for mesh currents for the circuit shown in figure



Sol:


By inspection,  $(12)I_1 + (-4)I_2 = 42$

$$(-4)I_1 + (10)I_2 = 10$$

$$I_1 = 4.42A$$

$$I_2 = 2.76A$$

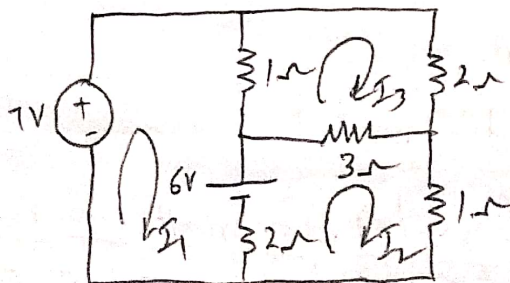Prob: For the circuit shown in figure, find the mesh currents.



Sol:


By inspection,  $(3)I_1 + (-2)I_2 + (-1)I_3 = 7-6$

$$(-2)I_1 + (6)I_2 + (-3)I_3 = 6$$

$$(-1)I_1 + (-3)I_2 + (6)I_3 = 0$$

$$I_1 = 3A, I_2 = 3A, I_3 = 2A$$

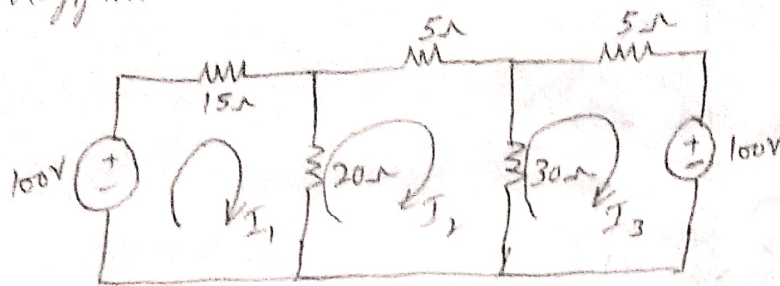Prob: Find the current in  $30\Omega$  resistance using mesh analysis for the circuit shown in the figure.



By inspection,  $(35)I_1 + (-20)I_2 + (-0)I_3 = 100$

$$(-20)I_1 + (55)I_2 + (-30)I_3 = 0$$

$$(-0)I_1 + (-30)I_2 + (35)I_3 = -100$$

$$I_1 = 1.942 \text{ A}$$

$$I_2 = -1.6 \text{ A}$$

$$I_3 = -4.22 \text{ A}$$

$$I_{30\Omega} = I_2 - I_3 = (-1.6) - (-4.22) = 2.62 \text{ A}$$

(↓)

Prob: Find the current in  $4\Omega$  resistance using mesh analysis for the circuit shown in the figure.



By inspection,  $(21)I_1 + (-5)I_2 + (-6)I_3 = 100$

$$(-5)I_1 + (12)I_2 + (-4)I_3 = -20$$

$$(-6)I_1 + (-4)I_2 + (11)I_3 = 10$$

$$I_1 = 7.34 \text{ A}$$


$$I_2 = 3.45 \text{ A}$$

$$I_3 = 6.17 \text{ A}$$

$$I_{4\Omega} = I_2 - I_3 = 3.45 - 6.17 = -2.72 \text{ A}$$

(←)  $I_{4\Omega} (\rightarrow) = I_2 - I_3 = 2.72 \text{ A}$

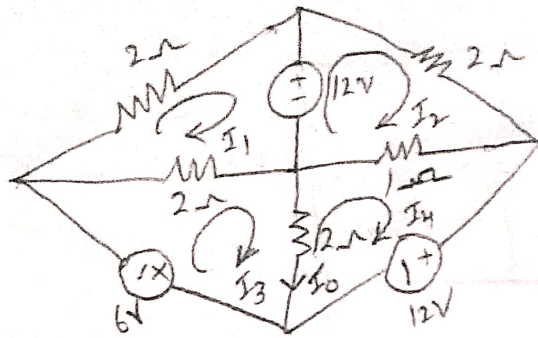Prob: In the circuit shown in figure, find  $I_0$  using mesh analysis.



Sol.

By inspection,

$$(4)I_1 + (-0)I_2 + (-2)I_3 + (-0)I_4 = -12 \quad \text{--- (1)}$$

$$(-0)I_1 + (3)I_2 + (-0)I_3 + (-1)I_4 = +12 \quad \text{--- (2)}$$

$$(-2)I_1 + (-0)I_2 + (4)I_3 + (-2)I_4 = -6 \quad \text{--- (3)}$$

$$(-0)I_1 + (-1)I_2 + (-2)I_3 + (3)I_4 = -12 \quad \text{--- (4)}$$

From equation (1),  $-2I_3 = -12 - 4I_1$

$$I_3 = 6 + 2I_1$$

Substitute for  $I_3$  in eq (2), (3) & (4)

$$\text{Eq (2)} \Rightarrow 3I_2 - I_4 = 12$$

$$\text{Eq (3)} \Rightarrow -2I_1 + 4(6 + 2I_1) - 2I_4 = -6$$

$$\text{Eq (4)} \Rightarrow -I_2 - 2(6 + 2I_1) + 3I_4 = -12$$

Solving the above equations,

$$(0)I_1 + (3)I_2 + (-1)I_4 = 12$$

$$(6)I_1 + (0)I_2 + (-2)I_4 = -30$$

$$(-4)I_1 + (-1)I_2 + (3)I_4 = 0$$

$$x = I_1 = -9A$$



$$y = I_2 = 0A$$

$$z = I_4 = -12A$$

$$I_3 = 6 + 2I_1 = -12A$$

$$I_0 = I_3 - I_4 = -12 - (-12) = 0A$$

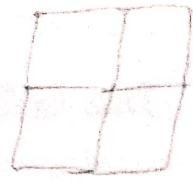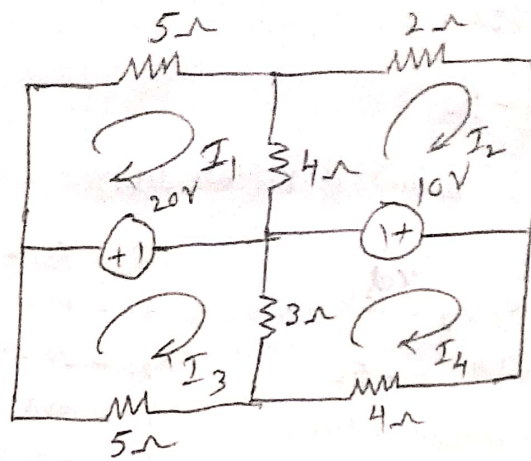Prob: Obtain the four mesh currents for the circuit shown in figure.



By inspection,

$$(9)I_1 + (-4)I_2 + (0)I_3 + (0)I_4 = 20 \quad \text{--- ①}$$

$$(-4)I_1 + (6)I_2 + (0)I_3 + (0)I_4 = -10 \quad \text{--- ②}$$

$$(0)I_1 + (0)I_2 + (8)I_3 + (-3)I_4 = -20 \quad \text{--- ③}$$

$$(0)I_1 + (0)I_2 + (-3)I_3 + (7)I_4 = 10 \quad \text{--- ④}$$

From equation ①,  $4I_2 = 9I_1 - 20$

$$I_2 = 2.25I_1 - 5$$

Substitute for  $I_2$  in eq ②, ③ & ④

$$\text{Eq ②} \Rightarrow -4I_1 + 6(2.25I_1 - 5) = -10$$

$$\text{Eq ③} \Rightarrow 8I_3 - 3I_4 = -20$$

$$\text{Eq ④} \Rightarrow -3I_3 + 7I_4 = 10$$

Solving the above equations,

$$(9.5)I_1 + (0)I_3 + (0)I_4 = 20$$

$$(0)I_1 + (8)I_3 + (-3)I_4 = -20$$

$$(0)I_1 + (-3)I_3 + (7)I_4 = 10$$

$$x = I_1 = 2.10 \text{ A}$$

$$y = I_3 = -2.34 \text{ A}$$

$$z = I_4 = 0.42 \text{ A}$$

$$I_2 = 2.25I_1 - 5$$

$$= 2.25 \times 2.10 - 5$$

$$= -0.275 \text{ A}$$

Prob: The mesh equations of a particular circuit are:

$$20I_1 - 10I_2 = 100$$

$$-10I_1 + 30I_2 = -50$$

Draw the circuit and insert the values of voltage sources and resistances.

Sol:

$$(20)I_1 + (-10)I_2 = 100$$

$$(-10)I_1 + (30)I_2 = -50$$

Procedure: 1) First note the common elements between meshes,  $R_{12} = 10\Omega$


2) The remaining resistance in the first mesh is  $R_{11} - R_{12} = 20 - 10 = 10\Omega$

The remaining resistance in the second mesh is  $R_{22} - R_{12} = 30 - 10 = 20\Omega$

3) Write the voltage source in the mesh 1,  $V_1 = 100V$  (Taking care of polarity)

Write the voltage source in the mesh 2,  $V_2 = -50V$  (Taking care of polarity)

4) Write clockwise mesh currents.

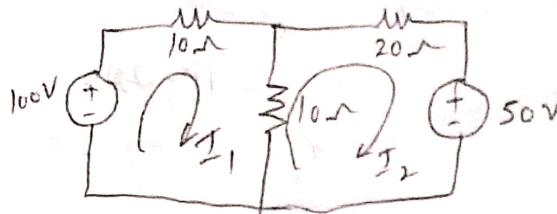

$$R_{12} = R_{21} = 10\Omega$$

$$R_{11} = 20\Omega$$

$$R_{22} = 30\Omega$$

$$V_1 = 100V$$

$$V_2 = -50V$$

(Multiply by given value by -)

Prob: The mesh equations of a particular circuit are:

$$11I_1 - 5I_2 = 50$$

$$-5I_1 + 27I_2 - 4I_3 = 0$$

$$-4I_2 + 8I_3 = 0$$


Draw the circuit.

Sol:

$$(11)I_1 + (-5)I_2 + (0)I_3 = 50$$

$$(-5)I_1 + (27)I_2 + (-4)I_3 = 0$$

$$(0)I_1 + (-4)I_2 + (8)I_3 = 0$$

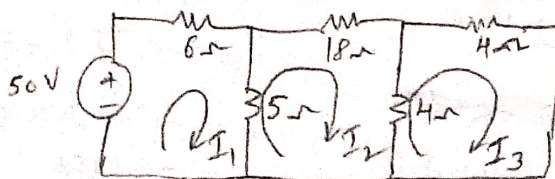

$$R_{12} = R_{21} = 5\Omega$$

$$R_{13} = R_{31} = 0\Omega$$

$$R_{23} = R_{32} = 4\Omega$$

$$R_{11} = 11\Omega, R_{22} = 27\Omega$$

$$R_{33} = 8\Omega$$

$$V_1 = 50V, V_2 = 0V$$

$$V_3 = 0V$$

When  $R_{13} = R_{31} = 0\Omega$ , the circuit can be written

as above. There is no common element between mesh 1 & 3.

Prob. The mesh equations of a particular circuit are:

$$2I_1 - 5I_2 - 6I_3 = 100$$

$$-5I_1 + 12I_2 - 4I_3 = -20$$

$$-6I_1 - 4I_2 + 11I_3 = 10$$

Draw the circuit.

Sol.

$$(2)I_1 + (-5)I_2 + (-6)I_3 = 100$$

$$(-5)I_1 + (12)I_2 + (-4)I_3 = -20$$

$$(-6)I_1 + (-4)I_2 + (11)I_3 = 10$$

$$R_{12} = R_{21} = 5\Omega$$


$$R_{13} = R_{31} = 6\Omega$$

$$R_{23} = R_{32} = 4\Omega$$

$$R_{11} = 21\Omega \quad V_1 = 100V$$

$$R_{22} = 12\Omega \quad V_2 = -20V$$

$$R_{33} = 11\Omega \quad V_3 = 10V$$

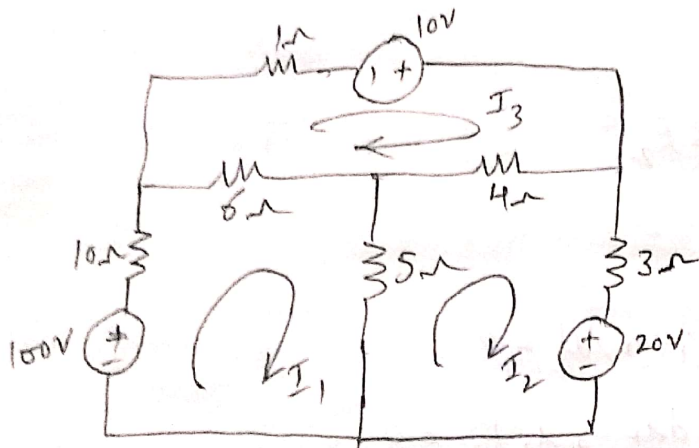

		3
1	✓	

not 

1	2	3
---	---	---

As  $R_{13} = R_{31}$   
it is not zero

# Loop Analysis (Mesh Analysis) (AC Excitation)

Note:

Time domain equations:

$$V = iR$$

$$V(t) = V_m \cos(\omega t \pm \phi)$$

R unit is  $\Omega$

$$V = L \frac{di}{dt}$$

$$i(t) = I_m \cos(\omega t \pm \phi)$$

L unit is H (henry)


C unit is F (farad)

V & i should be in lowercase

$$V = \frac{1}{C} \int i dt$$


(Voltage source & current source expressions)

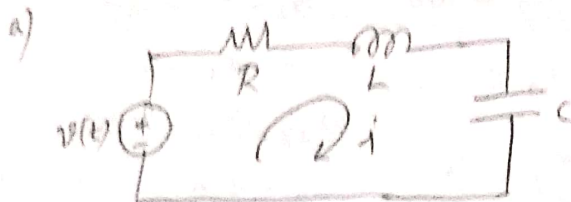Prob: Write down the KVL equations in time domain for the following circuits



$$-V(t) + iR + L \frac{di}{dt} + \frac{1}{C} \int i dt = 0$$

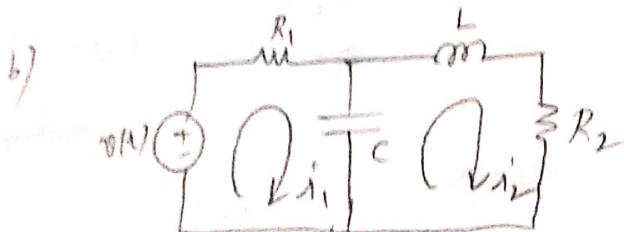
$$iR + L \frac{di}{dt} + \frac{1}{C} \int i dt = V(t)$$



KVL to loop 1:  $-V(t) + i_1 R_1 + \frac{1}{C} \int (i_1 - i_2) dt = 0$

KVL to loop 2:  $\frac{1}{C} \int (i_2 - i_1) dt + L \frac{di_2}{dt} + i_2 R_2 = 0$

c)

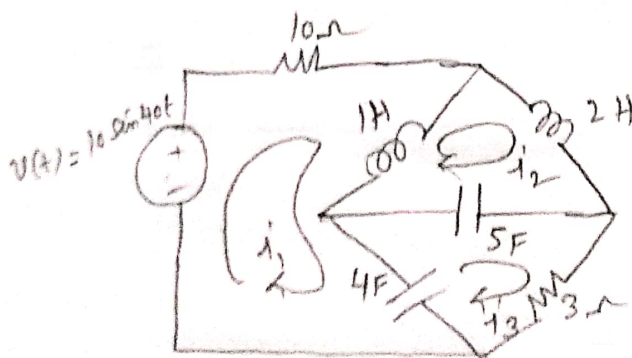


KVL to loop 1:  $-10 \sin 40t + 10 i_1 + \frac{1}{4} \frac{d}{dt} (i_1 - i_2) + \frac{1}{4} \int (i_1 - i_3) dt = 0$

KVL to loop 2:  $\frac{1}{4} \frac{d}{dt} (i_2 - i_1) + 2 \frac{d}{dt} (i_2 - i_1) + \frac{1}{5} \int (i_2 - i_3) dt = 0$

KVL to loop 3:  $\frac{1}{4} \int (i_3 - i_1) dt + \frac{1}{5} \int (i_3 - i_2) dt + 3 i_3 = 0$

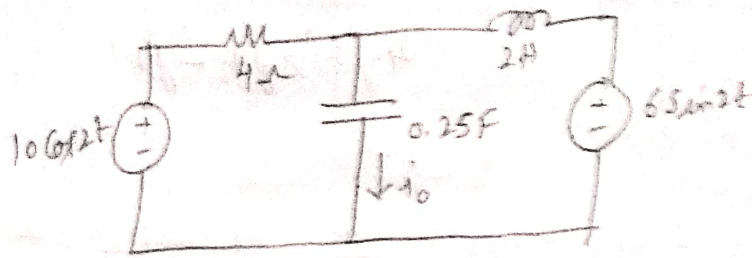
Prob: Solve for  $i_0$  using mesh analysis for the circuit shown in figure.



Sol: The given circuit is in time domain. It is converted to frequency domain (AC). Both the sources should be in 'cos' or 'sin'. From 'sin' to 'cos' subtract  $90^\circ$  from angle.

	Time domain	Frequency domain
$Z \rightarrow$ impedance		
$R \rightarrow$ Resistance		
$X_L \rightarrow$ inductive reactance		
$X_C \rightarrow$ capacitive reactance		
	$10 \cos 2t$	$10 \angle 0$
	$6 \sin 2t$	$6 \angle 0 \Rightarrow 6 \angle 0 - 90 = 6 \angle -90$
	$4 \Omega$	$4 \Omega$
	$2H$	$+jX_L \Rightarrow +j\omega L \Rightarrow +j \times 2 \times 2 = +j4 \Omega$
	$0.25F$	$-jX_C \Rightarrow -j \frac{1}{\omega C} \Rightarrow -j \frac{1}{2 \times 0.25} = -j2 \Omega$

} Now both the sources are in cos

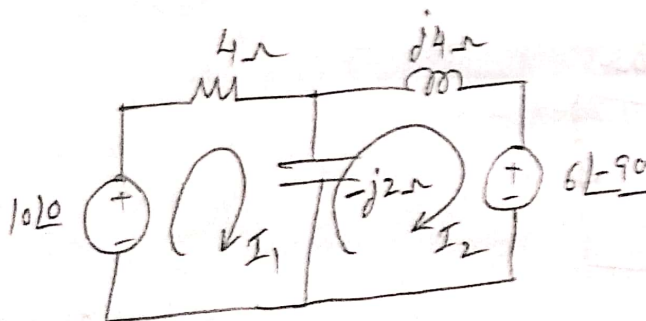

By inspection method,  $[Z][I] = [V]$

$$z_{11} I_1 + z_{12} I_2 = v_1$$

$$(4 - j2) I_1 + (+j2) I_2 = 10 \angle 0$$

$$z_{21} I_1 + z_{22} I_2 = v_2$$

$$(+j2) I_1 + (j2) I_2 = -6 \angle -90$$

off-diagonal we have to multiply the element by '-'. So  $-(-j2) = +j2$

By Cramer's rule

Keep calculator in complex & degree mode

$$I_1 = \frac{\begin{vmatrix} 10 \angle 0 & j2 \\ -6 \angle -90 & j2 \end{vmatrix}}{\begin{vmatrix} (4 - j2) & j2 \\ j2 & j2 \end{vmatrix}} = \frac{10 \times j2 + 6 \angle -90 \times j2}{(4 - j2) \times j2 - j2 \times j2} = \frac{(12 + j20)}{(8 + j8)}$$

$$I_1 = 2 + j0.5 = 2.06 \angle 14.03^\circ \text{ A (In frequency domain)}$$

$$i_0 = 2.06 \cos(2t + 14.03^\circ) \text{ A (In time domain)}$$

$$I_2 = \frac{\begin{vmatrix} (4-j2) & 10\angle 0 \\ j2 & -6\angle -90 \end{vmatrix}}{\begin{vmatrix} (4-j2) & j2 \\ j2 & j2 \end{vmatrix}} = \frac{-(4-j2) \times 6\angle -90 - j2 \times 10}{(8+j8)}$$

(No change in  $\angle$ )

Note: In the numerator shift the '-' sign to  $-(4-j2) \times 6\angle -90$  or  $-6\angle -90 = +6\angle -90 \pm 180$   
 If we write  $(4-j2) \times -6\angle -90$  calculator will show Math Error  
 negative magnitude  $= 6\angle 90$


$$I_2 = \frac{(12+j4)}{(8+j8)} = 1-j0.5 = 1.118\angle -26.56^\circ \text{ A (frequency domain)}$$

$$i_2 = 1.118 \cos(2t - 26.56^\circ) \text{ (Time domain)}$$


$$I_0 = I_1 - I_2 = (2+j0.5) - (1-j0.5) = (1+j1) = 1.414\angle 45^\circ \text{ A (frequency domain)}$$

$$i_0 = 1.414 \cos(2t + 45^\circ) \text{ (Time domain)}$$

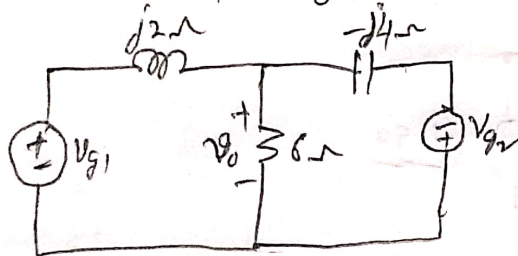
Prob. Solve the following example by mesh current method given  $v_{g1} = 10\cos(5000t + 53.13^\circ)$   
 $v_{g2} = 8\sin 5000t$ . Find  $v_0$ .



Sol.

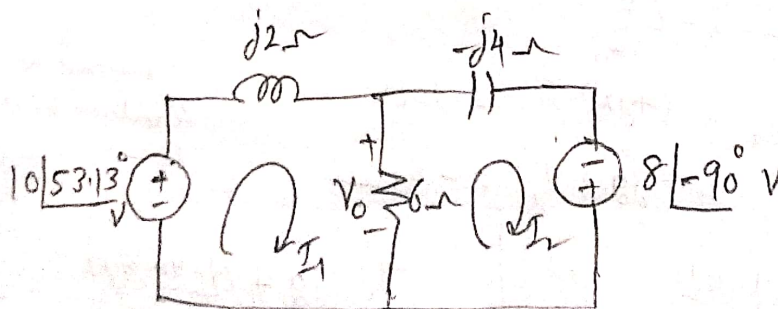

Note: If it is given as

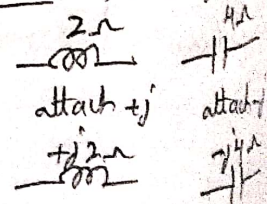

By inspection

method

$$(6+j2)I_1 + (-6)I_2 = 10\angle 53.13^\circ$$

$$(-6)I_1 + (6-j4)I_2 = 8\angle -90^\circ$$

By Cramer's rule,  $I_1 = \frac{\begin{vmatrix} 10\angle 53.13 & -6 \\ 8\angle -90 & (6-j4) \end{vmatrix}}{\begin{vmatrix} (6+j2) & -6 \\ -6 & (6-j4) \end{vmatrix}} = \frac{10\angle 53.13 \times (6-j4) + 6 \times 8\angle -90}{(6+j2)(6-j4) - 6 \times 6}$

$$I_1 = \frac{(68-j24)}{(8-j12)} = 4+j3 = 5\angle 36.86^\circ A$$

$$i_1 = 5\cos(5000t + 36.86^\circ) \text{ (Time domain)}$$

$$I_2 = \frac{\begin{vmatrix} (6+j2) & 10\angle 53.13 \\ -6 & 8\angle -90 \end{vmatrix}}{(8-j12)} = \frac{(6+j2) \times 8\angle -90 + 6 \times 10\angle 53.13}{(8-j12)}$$

$$I_2 = \frac{52}{(8-j12)} = 2+j3 = 3.6\angle 56.3^\circ$$

$$i_2 = 3.6\cos(5000t + 56.3^\circ)$$


$$V_0 = 6 \times (I_1 - I_2)$$

$$V_0 = 6 \times (4+j3 - 2-j3) = 12V$$

$$v_0 = 12\cos(5000t)$$

prob. For the network shown in figure find  $V_{AB}$  &  $V_{BC}$  using mesh analysis

Ex 1

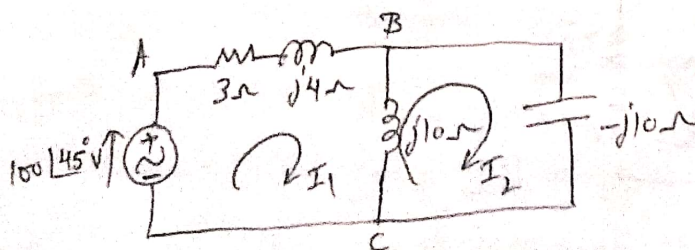

Note:



If voltage source is shown with an arrow mark, mark + polarity for the tip of arrow mark

By inspection,  $(3+j14)I_1 + (-j10)I_2 = 100\angle 45^\circ$

$(-j10)I_1 + (0)I_2 = 0$

By Cramer's rule,  $I_1 = \frac{\begin{vmatrix} 100\angle 45^\circ & -j10 \\ 0 & 0 \end{vmatrix}}{\begin{vmatrix} (3+j14) & -j10 \\ -j10 & 0 \end{vmatrix}} = \frac{0}{0} = 0A$

$I_2 = \frac{\begin{vmatrix} (3+j14) & 100\angle 45^\circ \\ -j10 & 0 \end{vmatrix}}{\begin{vmatrix} (3+j14) & -j10 \\ -j10 & 0 \end{vmatrix}}$

$I_2 = \frac{j10 \times 100\angle 45^\circ}{-j10 \times j10} = \frac{(-707.10 + j707.10)}{100}$

$I_2 = -7.071 + j7.071 = 10\angle 135^\circ A$


$V_{AB} = (3+j14) \times I_1 = (3+j14) \times 0 = 0$

$V_{BC} = j10 \times (I_1 - I_2) = j10 \times -10\angle 135^\circ = -j10 \times 10\angle 135^\circ = 70.71 + j70.71$

$V_{BC} = 100\angle 45^\circ$

Prob. Find the power output of the voltage source in the circuit shown in the figure and also determine the power in the circuit resistors using mesh analysis

Sol:

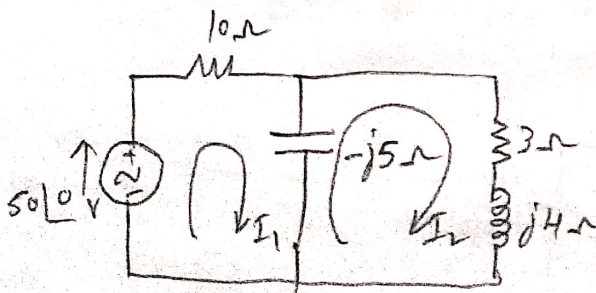

By inspection method,

$$(10-j5)I_1 + (+j5)I_2 = 50\angle 0^\circ$$

$$(+j5)I_1 + (3-j1)I_2 = 0$$

By Cramer's rule, 
$$I_1 = \frac{\begin{vmatrix} 50\angle 0^\circ & j5 \\ 0 & (3-j1) \end{vmatrix}}{\begin{vmatrix} (10-j5) & j5 \\ j5 & (3-j1) \end{vmatrix}} = \frac{50 \times (3-j1)}{(10-j5) \times (3-j1) - j5 \times j5}$$

$$I_1 = \frac{(150-j50)}{(50-j25)} = 2.8 + j0.4 = 2.828 \angle 8.13^\circ$$

$$I_2 = \frac{\begin{vmatrix} (10-j5) & 50\angle 0^\circ \\ j5 & 0 \end{vmatrix}}{(50-j25)} = \frac{-j5 \times 50}{(50-j25)} = \frac{-j250}{(50-j25)}$$

$$I_2 = 2-j4 = 4.47 \angle -63.43^\circ$$

Take only  
Magnitude of voltage & current

Power delivered by voltage source,  $P_{\text{Source}} = |V| |I_1| = 50 \times 2.828 = 141.4 \text{ W}$

$$P_{10\Omega} = |I_1|^2 \times 10 = 2.828^2 \times 10 = 80 \text{ W}$$


$$P_{3\Omega} = |I_2|^2 \times 3 = 4.47^2 \times 3 = 60 \text{ W}$$

$$P_{j4\Omega} = 0 \text{ W}$$

$$P_{-j5\Omega} = 0 \text{ W}$$

} pure inductor & pure capacitor  
does not consume any power.

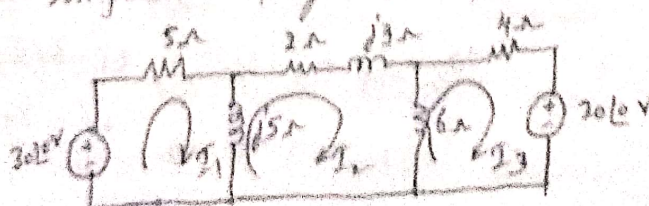Prob. The network shown in the figure contains two voltage sources. Find the current in the  $(2+j3)\Omega$  impedance using loop analysis.



By inspection method,

$$(5+j5)I_1 + (-j5)I_2 + (0)I_3 = 30\angle 0$$

$$(-j5)I_1 + (8+j8)I_2 + (-6)I_3 = 0$$

$$(0)I_1 + (-6)I_2 + (10)I_3 = -20\angle 0$$

Current through  $(2+j3)\Omega$  is  $I_2$ . We need to find only  $I_2$  not  $I_1$  &  $I_3$ .

By Cramer's rule,


$$I_2 = \frac{\begin{vmatrix} (5+j5) & 30\angle 0 & 0 \\ -j5 & 0 & -6 \\ 0 & -20\angle 0 & 10 \end{vmatrix}}{\begin{vmatrix} (5+j5) & -j5 & 0 \\ -j5 & (8+j8) & -6 \\ 0 & -6 & 10 \end{vmatrix}} = \frac{(5+j5) \times -6 \times 20 - 30 \times -j5 \times 10}{(5+j5) \times \{ (8+j8) \times 10 - 6 \times 6 \} + j5 \times 10 \times -j5}$$

$$I_2 = \frac{(-600 + j900)}{(5+j5) \times (44+j80) + 250} = \frac{(-600 + j900)}{(70 + j620)}$$

$$I_2 = 1.325 + j1.117 = 1.73\angle 40.13^\circ \text{ A}$$

Prob: In the network shown in figure determine  $V_2$  such that the current in the impedance  $(2+j3)\Omega$  is zero. Use mesh analysis.

Sol:

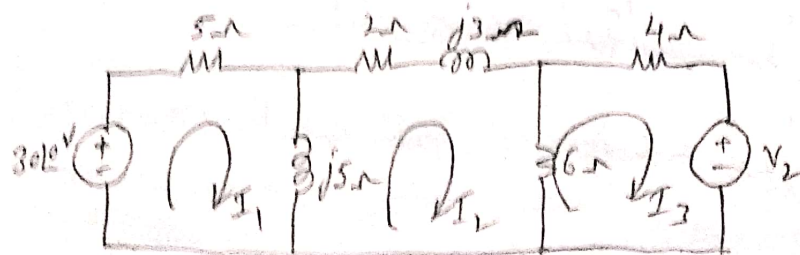

By inspection method,

$$(5+j5)I_1 + (-j5)I_2 + (0)I_3 = 30\angle 0$$

$$(-j5)I_1 + (8+j8)I_2 + (-6)I_3 = 0$$

$$(0)I_1 + (-6)I_2 + (10)I_3 = -V_2$$

Given  $I_{(2+j3)\Omega} = 0$  which means  $I_2 = 0$

By Cramer's rule,

$$I_2 = \frac{\begin{vmatrix} (5+j5) & 30 & 0 \\ -j5 & 0 & -6 \\ 0 & -V_2 & 10 \end{vmatrix}}{\begin{vmatrix} (5+j5) & -j5 & 0 \\ -j5 & (8+j8) & -6 \\ 0 & -6 & 10 \end{vmatrix}} = 0$$

$$\begin{vmatrix} (5+j5) & 30 & 0 \\ -j5 & 0 & -6 \\ 0 & -V_2 & 10 \end{vmatrix} = 0$$

$$(5+j5) \times -6V_2 - 30 \times -j5 \times 10 = 0$$

$$(5+j5) \times -6V_2 + j1500 = 0$$


$$(5+j5) \times -6V_2 = -j1500$$

$$V_2 = \frac{-j1500}{-6 \times (5+j5)} = \frac{+j1500}{(+30+j30)}$$

$$V_2 = 25 + j25 = 35.35 \angle 45^\circ$$

Prob. Use loop analysis to determine Voltage 'V' such that current through  $(4+j3)\Omega$  is zero.

Sol:

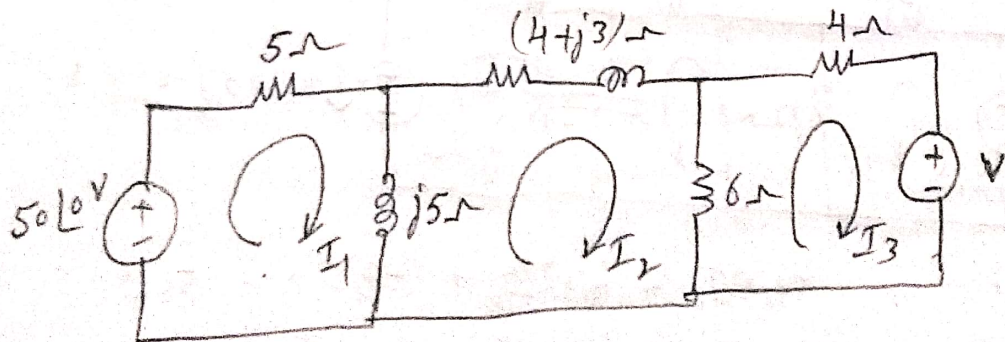

By inspection method

$$(5+j5)I_1 + (-j5)I_2 + (-0)I_3 = 50\angle 0$$

$$(-j5)I_1 + (10+j8)I_2 + (-6)I_3 = 0$$

$$(-0)I_1 + (-6)I_2 + (10)I_3 = -V$$

Given  $I_4 + j3I_2 = 0$  which means  $I_2 = 0$

$$\begin{vmatrix} (5+j5) & 50\angle 0 & 0 \\ -j5 & 0 & -6 \\ 0 & -V & 10 \end{vmatrix} = 0$$

or

$$(5+j5) \times -6V - 50 \times -j5 \times 10 = 0$$

$$(5+j5) \times -6V + j2500 = 0$$


$$(5+j5) \times -6V = -j2500$$

$$V = \frac{-j2500}{(5+j5) \times -6} = \frac{-j2500}{(-30-j30)}$$

$$V = 41.66 + j41.66$$

$$V = 58.92 \angle 45$$

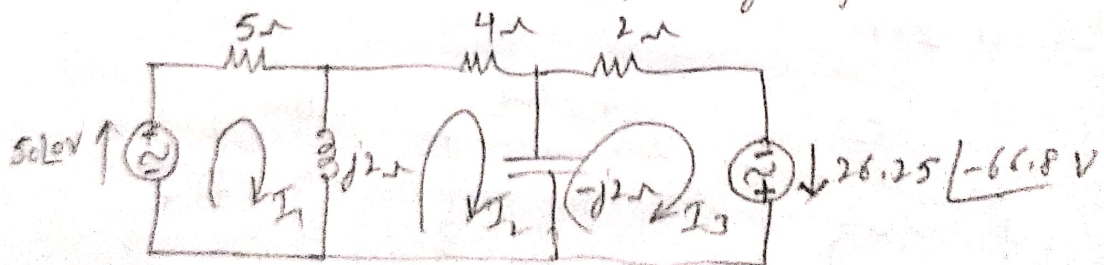Prob. Find Current through  $4\Omega$  resistor by using loop current method



By inspection

$$(5+j2)I_1 + (-j2)I_2 + (-0)I_3 = 50\angle 0$$

$$(-j2)I_1 + (4)I_2 + (+j2)I_3 = 0$$

$$(-0)I_1 + (+j2)I_2 + (2+j2)I_3 = 26.25 \angle -66.8$$

Current through  $4\Omega$  is  $I_2$ .

$$I_2 = \frac{\begin{vmatrix} (5+j2) & 50 & 0 \\ -j2 & 0 & j2 \\ 0 & 26.25 \angle -66.8^\circ & (2-j2) \end{vmatrix}}{D\delta} = \frac{(5+j2) \times -j2 \times 26.25 \angle -66.8^\circ - 50 \times -j2 \times (2-j2)}{D\delta}$$

$$I_2 = \frac{(-200 - j200) + (200 + j200)}{D\delta} = 0 \text{ A}$$

prob: The mesh equation of a given network are:

$$(8-j2)I_1 - 3I_2 = 10 \angle 30^\circ$$

$$-3I_1 + (8+j5)I_2 - 5I_3 = 0$$

$$-5I_2 + (7-j2)I_3 = 0$$

Draw the network satisfying the above equations.

Sol:

$$(8-j2)I_1 + (-3)I_2 + (0)I_3 = 10 \angle 30^\circ$$

$$(-3)I_1 + (8+j5)I_2 + (-5)I_3 = 0$$

$$(0)I_1 + (-5)I_2 + (7-j2)I_3 = 0$$

Multiply by '-' for off diagonal elements,

$$Z_{12} = Z_{21} = 3\Omega$$

$$Z_{13} = Z_{31} = 0$$

$$Z_{23} = Z_{32} = 5\Omega$$

$$V_1 = 10 \angle 30^\circ$$


$$0$$

$$0$$

$$Z_{11} = (8-j2)$$

$$Z_{22} = (8+j5)$$

$$Z_{33} = (7-j2)$$

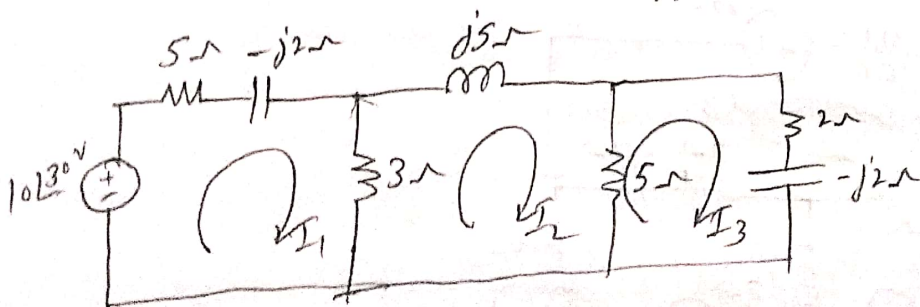


Prob. Draw a network for the following mesh equations in matrix form

$$\begin{bmatrix} 5+j5 & -j5 & 0 \\ -j5 & 8+j8 & -6 \\ 0 & -6 & 10 \end{bmatrix} \begin{bmatrix} I_1 \\ I_2 \\ I_3 \end{bmatrix} = \begin{bmatrix} 30\angle 0 \\ 0 \\ -20\angle 0 \end{bmatrix}$$

Sol:
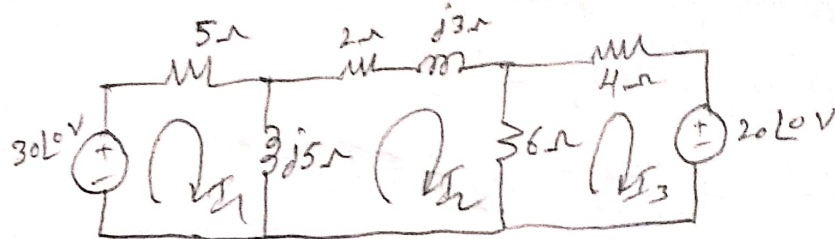
$$\begin{aligned} Z_{12} = Z_{21} &= +j5\Omega & Z_{11} &= 5+j5 & V_1 &= 30\angle 0 \\ Z_{13} = Z_{31} &= 0\Omega & Z_{22} &= 8+j8 & V_2 &= 0 \\ Z_{23} = Z_{32} &= 6\Omega & Z_{33} &= 10 & V_3 &= -20\angle 0 \end{aligned}$$





Prob: From the following representation of the matrix form of loop equations, draw the corresponding network.

$$\begin{bmatrix} 7+j3 & -j5 & -5 \\ -j5 & 12+j3 & -2+j2 \\ -5 & -2+j2 & 17-j2 \end{bmatrix} \begin{bmatrix} I_1 \\ I_2 \\ I_3 \end{bmatrix} = \begin{bmatrix} 10\angle 0 \\ -15\angle 0 \\ -25\angle 0 \end{bmatrix}$$



Sol:

$$\begin{aligned} Z_{11} = Z_{21} &= j5 & Z_{11} &= 7+j3 & V_1 &= 10\angle 0 \\ Z_{13} = Z_{31} &= 5 & Z_{22} &= 12+j3 & V_2 &= -15\angle 0 \\ Z_{23} = Z_{32} &= 2-j2 & Z_{33} &= 17-j2 & V_3 &= -25\angle 0 \end{aligned}$$

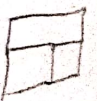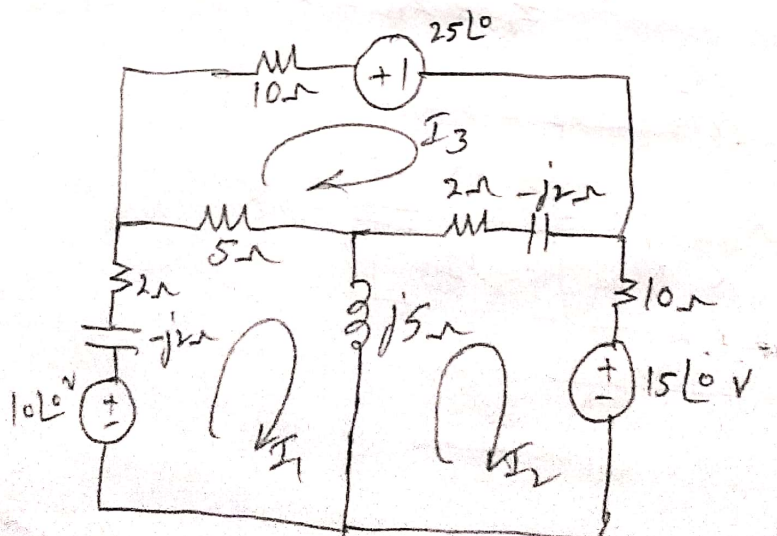Since  $Z_{13}$  is not zero the n/w looks like



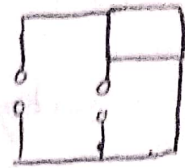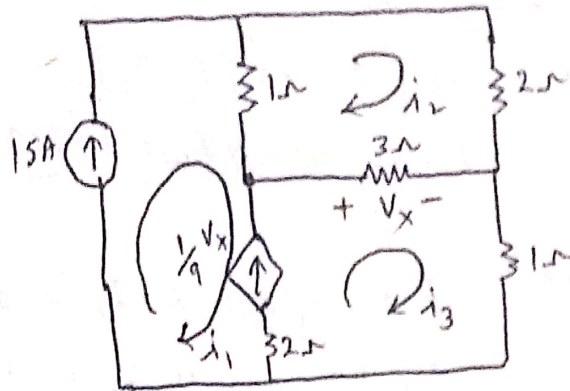Find the three unknown currents in the circuit shown in figure using mesh Analysis. (8 Marks)



$$V_x = 3(i_3 - i_2)$$

KCL to non essential mesh 1:  $i_1 = +15$

KCL to non essential mesh 3:  $i_3 - i_1 = \frac{1}{9} \left\{ \frac{V_x}{3} (i_3 - i_2) \right\} \Rightarrow 3(i_3 - i_1) = i_3 - i_2$

KVL to essential mesh 2:  $1(i_2 - i_1) + 2i_2 + 3(i_2 - i_3) = 0$

Sorting the above equations:

$$(1)i_1 + (0)i_2 + (0)i_3 = 15$$

$$(-3)i_1 + (1)i_2 + (2)i_3 = 0$$

$$(-1)i_1 + (6)i_2 + (-3)i_3 = 0$$



$$i_1 = 15A$$

$$i_2 = 11A$$

$$i_3 = 17A$$

c. Find the loop currents  $i_1$ ,  $i_2$  and  $i_3$  using mesh analysis for the network shown in figure. (6 Marks)

Sol:

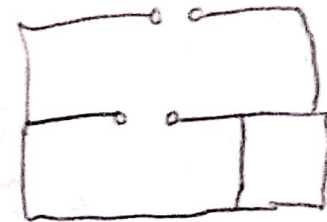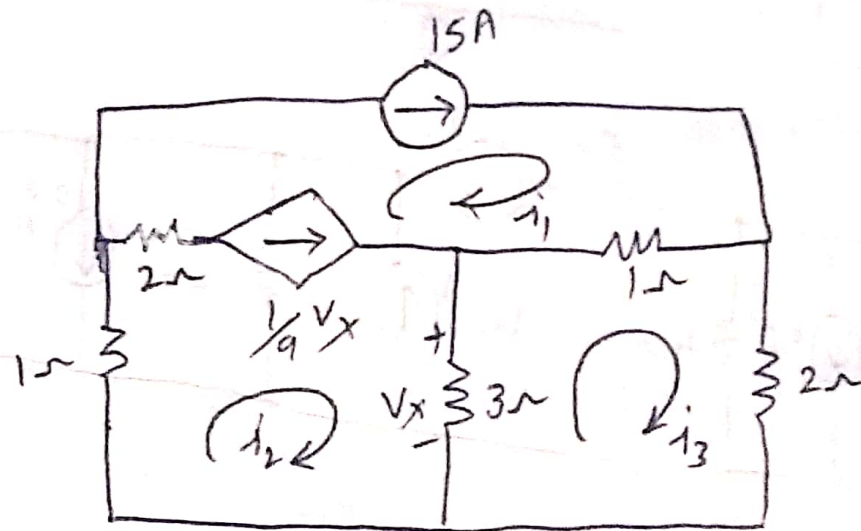

$$V_x = 3(i_2 - i_3)$$

KCL to non essential mesh 1 :  $i_1 = 15$

KCL to non essential mesh 2 :  $i_2 - i_1 = \frac{1}{9} \left\{ \underset{\substack{\longleftarrow \\ V_x}}{3(i_2 - i_3)} \right\} \Rightarrow 3(i_2 - i_1) = i_2 - i_3$

KVL to essential mesh 3 :  $3(i_3 - i_2) + 1(i_3 - i_1) + 2i_3 = 0$

$$(1)i_1 + (0)i_2 + (0)i_3 = 15$$

$$(-3)i_1 + (2)i_2 + (1)i_3 = 0$$



$$(-1)i_1 + (-3)i_2 + (6)i_3 = 0$$

$$i_1 = 15 A$$

$$i_2 = 17 A$$

$$i_3 = 11 A$$

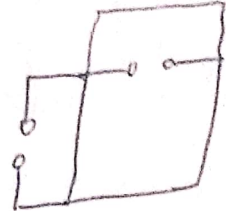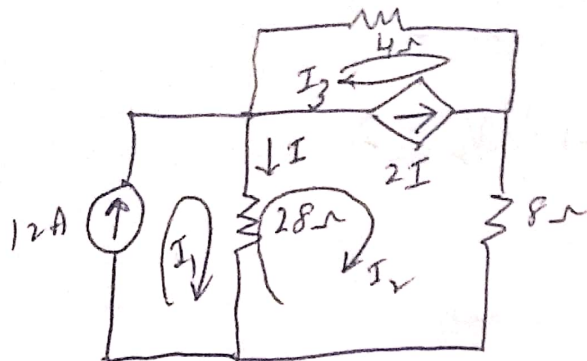Find the current  $I$  Using mesh Analysis for the Circuit shown in figure. (8 marks) 47



$$I = I_1 - I_2$$

KCL to nonessential mesh 1:  $I_1 = 12$

KCL to supermesh 2 & 3:  $I_2 - I_3 = 2(I_1 - I_2)$   
 $\xrightarrow{I}$

KVL to supermesh 2 & 3:  $28(I_2 - I_1) + 4I_3 + 8I_2 = 0$

$$(1)I_1 + (0)I_2 + (0)I_3 = 12$$

$$(-2)I_1 + (3)I_2 + (-1)I_3 = 0$$

$$(-28)I_1 + (36)I_2 + (4)I_3 = 0$$

$$I_1 = 12A$$


$$I_2 = 9A$$

$$I_3 = 3A$$

$$I = I_1 - I_2 = 12 - 9 = 3A$$

c. Use mesh analysis to determine the branch currents in the network indicated in the figure (6 marks)

Sol:

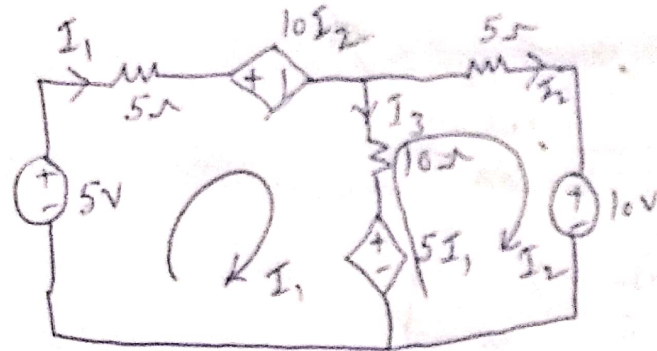

$$\text{KVL to essential mesh 1: } -5 + 5I_1 + 10I_2 + 10(I_1 - I_2) + 5I_1 = 0$$

$$\text{KVL to essential mesh 2: } -5I_1 + 10(I_2 - I_1) + 5I_2 + 10 = 0$$

$$(20)I_1 + (0)I_2 = 5$$



$$(-15)I_1 + (15)I_2 = -10$$

$$I_1 = 0.25 \text{ A}$$

$$I_2 = -0.416 \text{ A}$$

$$I_3 = I_1 - I_2 = 0.25 + 0.416 \\ = 0.666 \text{ A}$$

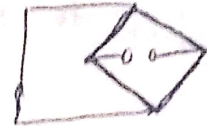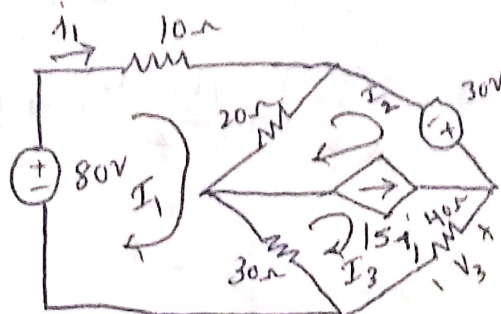a. Determine Voltage  $V_3$  for the circuit shown in figure using mesh analysis method. (8 Marks)



KCL to supermesh 2 & 3:  $i_1 = I_1$   
 $I_3 - I_2 = 15I_1 \rightarrow i_1$

KVL to supermesh 2 & 3:  $30(I_3 - I_1) + 20(I_2 - I_1) - 30 + 40I_3 = 0$

KVL to essential mesh 1:  $-80 + 10I_1 + 20(I_1 - I_2) + 30(I_1 - I_3) = 0$

$$(-15)I_1 + (-1)I_2 + (1)I_3 = 0$$

$$(-50)I_1 + (20)I_2 + (70)I_3 = 30$$

$$(60)I_1 + (-20)I_2 + (-30)I_3 = 80$$

$$I_1 = 0.5838 \text{ A}$$


$$I_2 = -6.15 \text{ A}$$

$$I_3 = 2.60 \text{ A}$$

$$V_3 = +40I_3 = 40 \times 2.6 = 104 \text{ V}$$

∴ The voltage  $V_3$  for the circuit is 104 V

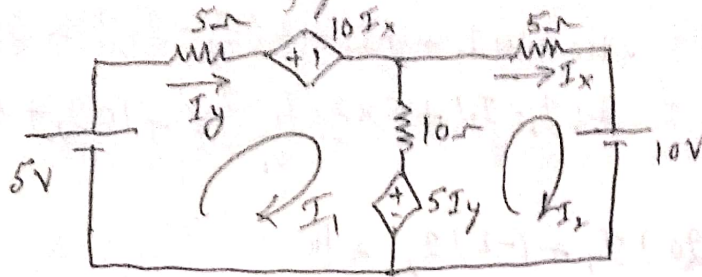Q. Using mesh analysis find the current through  $10\Omega$  resistor in the network shown in the figure.



Sol:

Control Variable,  $I_x = +I_2$

$I_y = +I_1$

KVL to essential mesh 1:  $-5 + 5I_1 + 10I_2 + 10(I_1 - I_2) + 5I_1 = 0$

KVL to essential mesh 2:  $-5I_1 + 10(I_2 - I_1) + 5I_2 + 10 = 0$

$$(20)I_1 + (0)I_2 = 5$$

$$(-15)I_1 + (15)I_2 = -10$$

$$I_1 = 0.25A$$


$$I_2 = -0.4166A$$

$$I_{10\Omega} = I_1 - I_2$$

$$= 0.25 - (-0.4166)$$


$$= 0.666A$$

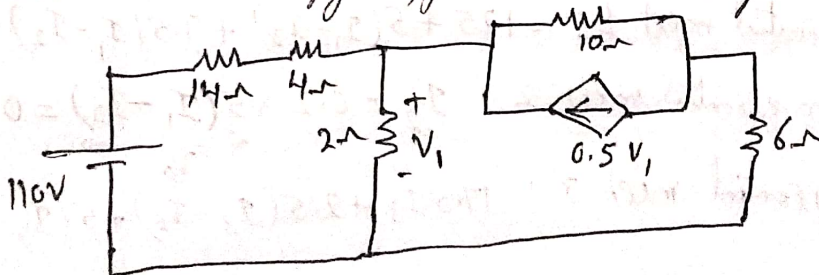6. For the network shown in the figure, find the current through  $4\Omega$  and  $6\Omega$  resistors.



Sol:

Using source transformation

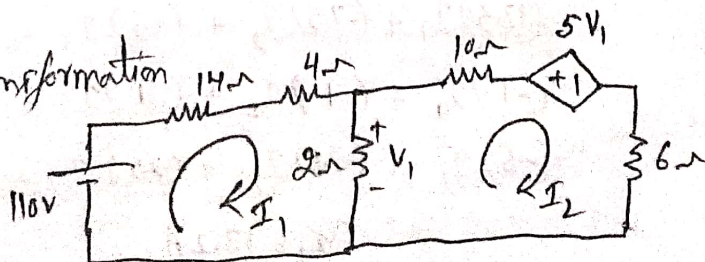

Control Variable,  $V_1 = 2(I_1 - I_2)$   
 entering '+' terminal

KVL to essential mesh 1:  $-110 + 14I_1 + 4I_1 + 2(I_1 - I_2) = 0$

KVL to essential mesh 2:  $2(I_2 - I_1) + 5 \times 2(I_1 - I_2) + 10I_2 + 6I_2 = 0$   
 $\xleftarrow{V_1}$

$$(20)I_1 + (-2)I_2 = 110$$

$$(-2)I_1 + (-2)I_2 = 0$$

$$I_1 = 5A$$



$$I_2 = -5A$$

$$I_{4A} = I_1 = 5A$$

$$I_{6A} = I_2 = -5A$$

Q. Find the mesh currents for the circuit shown in figure.

Sol:

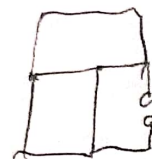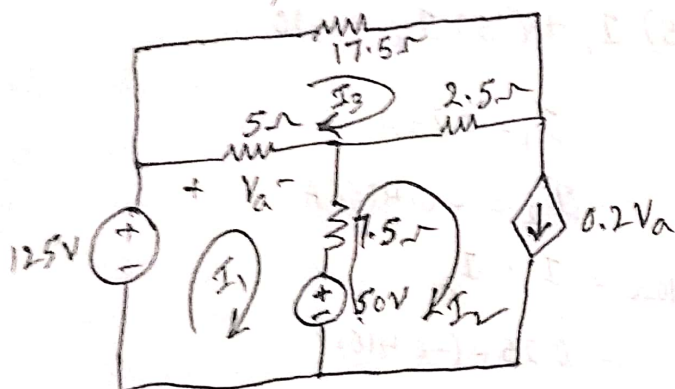

Control Variable,  $V_a = 5(I_1 - I_3)$   
 entering '+'

KVL to essential mesh 1:  $-125 + 5(I_1 - I_3) + 7.5(I_1 - I_2) + 50 = 0$

KCL to non-essential mesh 2:  $I_2 = 0.2 \times 5(I_1 - I_3)$   
 $\xleftarrow{V_a}$

KVL to essential mesh 3:  $17.5I_3 + 2.5(I_3 - I_2) + 5(I_3 - I_1) = 0$

$$(12.5)I_1 + (-7.5)I_2 + (-5)I_3 = 75$$

$$(-1)I_1 + (-1)I_2 + (1)I_3 = 0$$


$$(-5)I_1 + (-2.5)I_2 + (25)I_3 = 0$$

$$I_1 = 13.2A$$

$$I_2 = 9.6A$$

$$I_3 = 3.6A$$

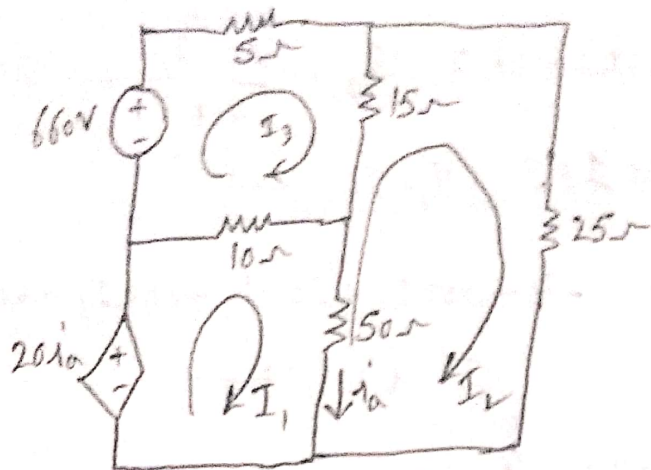Q. Find  $i_a$  in the circuit shown in figure using mesh analysis



Sol:

Control Variable,  $i_a = I_1 - I_2$

KVL to essential mesh 1:  $-20(I_1 - I_2) + 10(I_1 - I_3) + 50(I_1 - I_2) = 0$

KVL to essential mesh 2:  $50(I_2 - I_1) + 15(I_2 - I_3) + 25I_2 = 0$

KVL to essential mesh 3:  $-660 + 5I_3 + 15(I_3 - I_2) + 10(I_3 - I_1) = 0$

$$(40)I_1 + (-30)I_2 + (-10)I_3 = 0$$

$$(-50)I_1 + (90)I_2 + (-15)I_3 = 0$$

$$(-10)I_1 + (-15)I_2 + (30)I_3 = 660$$



$$I_1 = 27A$$

$$I_2 = 22A$$

$$I_3 = 42A$$

$$i_a = I_1 - I_2 = 27 - 22 = 5A$$

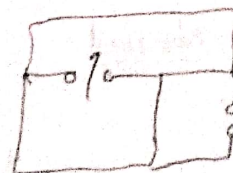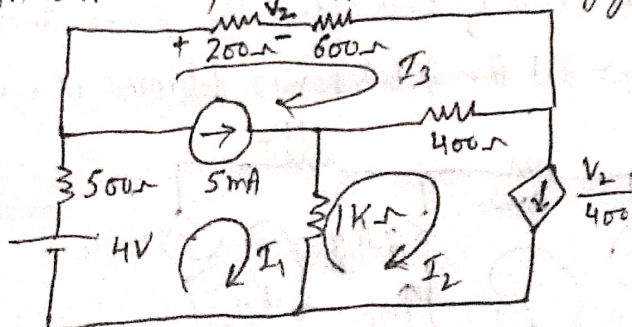Q. Solve for mesh currents for the circuit shown in figure. Find the power supplied by 4V



Control Variable,  $V_2 = +200 I_3$

KCL to non-essential mesh 2:  $I_2 = \frac{200 I_3}{400} \Rightarrow 2 I_2 = I_3$

KCL to supermesh 1 & 3:  $I_1 - I_3 = 5 \times 10^{-3}$

KVL to supermesh:  $-4 + 500 I_1 + 200 I_3 + 600 I_3 + 400(I_3 - I_2) + 1K(I_1 - I_2) = 0$

(0)  $I_1 + (2) I_2 + (-1) I_3 = 0$

(1)  $I_1 + (0) I_2 + (-1) I_3 = 5 \times 10^{-3}$

(1500)  $I_1 + (-1400) + (1200) I_3 = 4$

$I_1 = 3.25 \text{ mA}$

$I_2 = -8.75 \times 10^{-4} \text{ A} = -0.875 \text{ mA}$

$I_3 = -1.75 \text{ mA}$

$P_{\text{absorbed}(4V)} = - \overset{\text{current entering (-ve terminal)}}{\uparrow} (V) (I_1)$



$= -(4) (3.25 \times 10^{-3})$

$= -0.013 \text{ W}$

$= -13 \text{ mW}$

$P_{\text{delivered}(4V)} = +13 \text{ mW}$

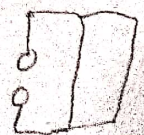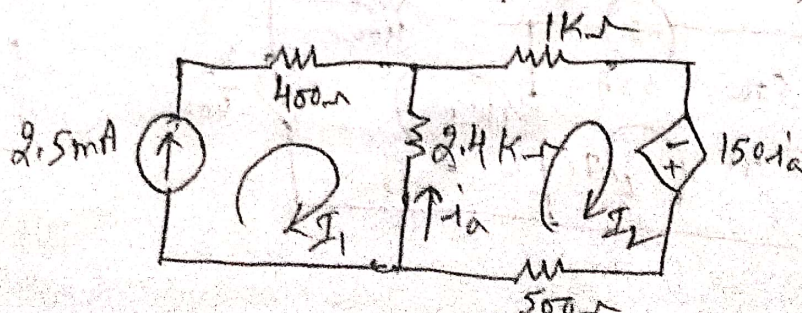6. Solve for mesh currents  $I_1$  &  $I_2$  and obtain the power delivered/absorbed by all the elements. Prove that the total power delivered is equal to total power absorbed.



Control Variable  $i_a = I_2 - I_1$

KCL for non-essential mesh 1,  $I_1 = 2.5 \times 10^{-3}$

KVL for essential mesh 2:  $2.4K(I_2 - I_1) + 1KI_2 - 150(I_2 - I_1) + 500I_2 = 0$

(1)  $I_1 + (0)I_2 = 2.5 \times 10^{-3}$

$(-2250)I_1 + (3750)I_2 = 0$

$I_1 = 2.5 \text{ mA}$

$i_a = I_2 - I_1 = -1 \text{ mA}$

$I_2 = 1.5 \text{ mA}$

Power will always be absorbed by resistances.

$P_{400\Omega} = I_1^2 \times 400 = (2.5 \times 10^{-3})^2 \times 400 = 2.5 \times 10^{-3} \text{ W}$

$P_{500\Omega} = I_2^2 \times 500 = (1.5 \times 10^{-3})^2 \times 500 = 1.125 \times 10^{-3} \text{ W}$

$P_{2.4K\Omega} = \frac{(I_2 - I_1)^2}{(I_1 - I_2)^2} \times 2.4 \times 10^3 = \left\{ \frac{(1.5 - 2.5) \times 10^{-3}}{(2.5 - 1.5) \times 10^{-3}} \right\}^2 \times 2.4 \times 10^3 = 2.4 \times 10^{-3} \text{ W}$

$P_{1K\Omega} = I_2^2 \times 1 \times 10^3 = (1.5 \times 10^{-3})^2 \times 1 \times 10^3 = 2.25 \times 10^{-3} \text{ W}$


$P_{\text{absorbed}} \left( \frac{1}{150} i_a \right) = -(V)(I_2) = -(150 i_a) \times I_2$   
 $= -(150 \times -1 \times 10^{-3}) \times 1.5 \times 10^{-3}$   
 $= 2.25 \times 10^{-4} \text{ W}$

$P_{\text{delivered}} \left( \frac{1}{2.5 \text{ mA}} \right)$

$= + (V_{cu}) I_1$

current  $I_1$  is coming out of '+' terminal

$= + (3.4) (2.5 \times 10^{-3})$

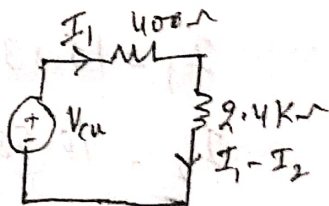

$V_{cu} \rightarrow$  voltage across current source

KVL:  $-V_{cu} + 400I_1 + 2.4(I_1 - I_2) \times 10^3 = 0$

$V_{cu} = 400 \times 2.5 \times 10^{-3} + 2.4 \times 10^3 \times (1 \times 10^{-3}) = 3.4 \text{ V}$

$P_{\text{delivered}} = 8.5 \times 10^{-3} \text{ W}$  (Total power delivered)


$P_{\text{absorbed}} = 2.5 \times 10^{-3} + 1.125 \times 10^{-3} + 2.4 \times 10^{-3} + 2.25 \times 10^{-3} + 2.25 \times 10^{-4} = 8.5 \times 10^{-3} \text{ W}$

$\therefore$  Total power delivered = Total power absorbed

Total power absorbed

Q. For the circuit shown in figure, find the power supplied by 5A source and the output of the dependent source using mesh analysis.

Sol:

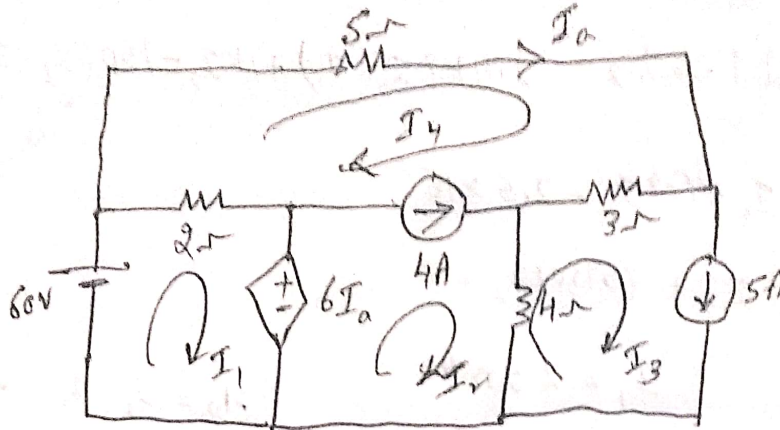

Sol:

Control Variable,  $I_a = I_4$

KCL for non-essential mesh 3:  $I_3 = 5$

KCL for supermesh 2 & 4:  $I_2 - I_4 = 4$

KVL for essential mesh 1:  $-60 + 2(I_1 - I_4) + 6I_4 = 0$

KVL for supermesh 2 & 4:  $-6I_4 + 2(I_4 - I_1) + 5I_4 + 3(I_4 - 5) + 4(I_2 - 5) = 0$

$$(0)I_1 + (1)I_2 + (-1)I_4 = 4$$

$$(2)I_1 + (0)I_2 + (4)I_4 = 60$$

$$(-2)I_1 + (4)I_2 + (4)I_4 = 35$$

$$I_1 = 16.833 \text{ A}$$

$$I_2 = 10.583 \text{ A}$$

$$I_4 = 6.583 \text{ A}$$


$$I_3 = 5 \text{ A}$$

$$P_{\text{delivered}}(5\text{A}) = +V_{cu} I_3$$

$$= +(-27.06)(5)$$

$$= -135.3 \text{ W}$$
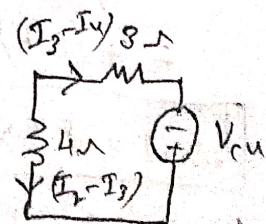
$$P_{\text{absorbed}}(5\text{A}) = +135.3 \text{ W}$$



$$3(I_3 - I_4) - V_{cu} - 4(I_2 - I_3) = 0$$

$$V_{cu} = 3(I_3 - I_4) - 4(I_2 - I_3)$$

$$V_{cu} = -27.06 \text{ V}$$




$$P_{\text{delivered}}(6V) = - (6I_a) \times (I_2 - I_1)$$

$\downarrow$   
 Voltage

$$= -6 \times 6.5833 \times (10.583 - 16.833)$$

$$= 246.87 \text{ W}$$

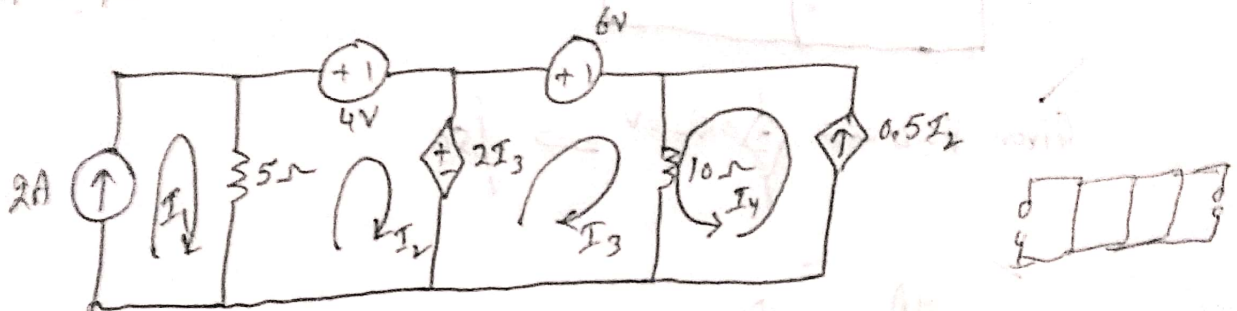a. Find the power delivered by the 6V source for the circuit shown in figure using loop analysis.



Sol:

KCL to non-essential mesh 1:  $I_1 = +2$

KCL to non-essential mesh 4:  $I_4 = +0.5I_2$

KVL to essential mesh 2:  $5(I_2 - 2) + 4 + 2I_3 = 0$

KVL to essential mesh 3:  $-2I_3 + 6 + 10(I_3 + I_4) = 0$

$$(-0.5)I_2 + (0)I_3 + (1)I_4 = 0$$

$$(5)I_2 + (2)I_3 + (0)I_4 = 6$$

$$(0)I_2 + (8)I_3 + (10)I_4 = -6$$

$$I_2 = 2 \text{ A}$$

$$I_1 = 2 \text{ A}$$

$$I_3 = -2 \text{ A}$$


$$I_4 = 1 \text{ A}$$

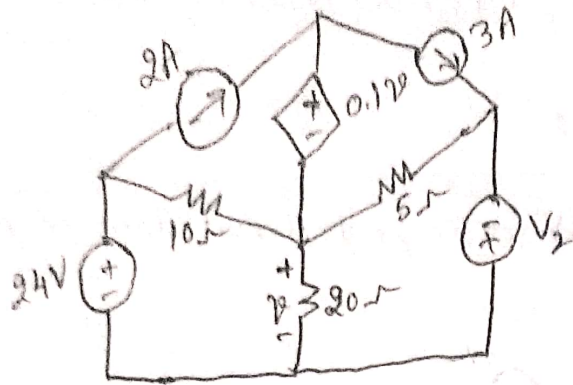
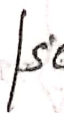
$$P_{\text{delivered}}(6V) = -(V)(I_3)$$




$$= -(6)(-2)$$

$$= +12 \text{ W}$$

Q. Use mesh analysis to determine What Value of  $V_2$  in the network shown in figure under  $V=0$ ,  $V$  is the Voltage across  $20\Omega$ .



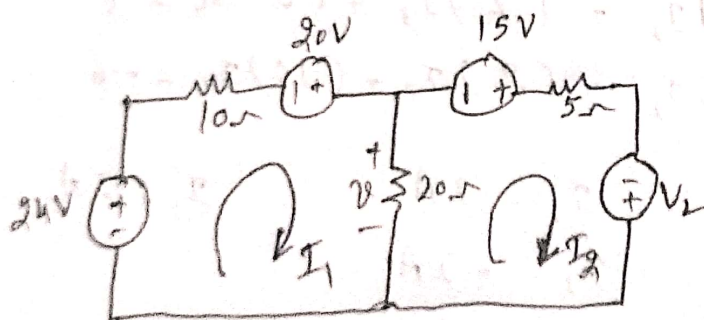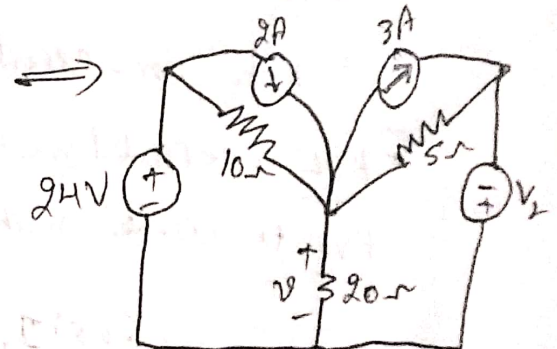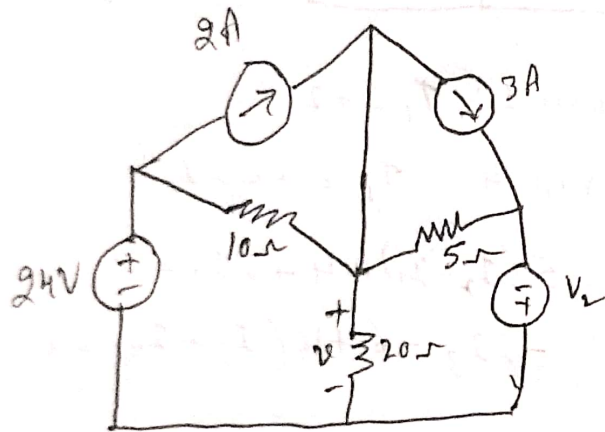Given  $V=0 \Rightarrow$    $0V=0V \Rightarrow$  



$$V=0 \Rightarrow 20(I_1 - I_2) = 0 \Rightarrow I_1 = I_2$$

KVL to loop 1:  $-24 + 10I_1 - 20 + 20(I_1 - I_2) = 0$

$$10I_1 = 44$$

$$I_1 = 4.4A$$

$$I_2 = 4.4A$$

KVL to loop 2:


$$20(\cancel{I_2} + I_1) - 15 + 5I_2 - V_2 = 0$$

$$V_2 = -15 + 5I_2$$



$$V_2 = -15 + 5 \times 4.4$$

$$V_2 = 7V$$

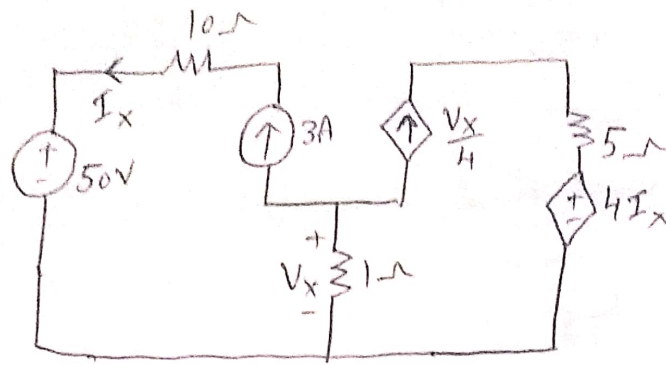1. c. Determine  $I_x$  and  $V_x$  for the circuit shown below using mesh analysis (7 marks)



Sol.

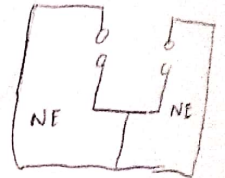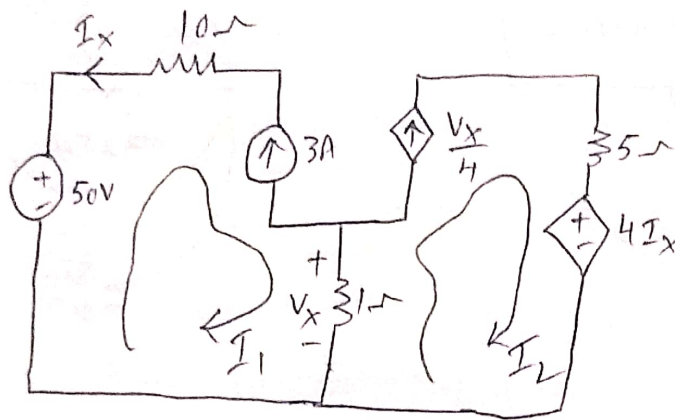

$$I_x = -I_1$$

$$V_x = +1(I_1 - I_2)$$

KCL equation for non essential mesh 1 :  $I_1 = -3$  — (1)

KCL equation for non essential mesh 2 :  $I_2 = \frac{+1(I_1 - I_2)}{4}$

$$4I_2 = I_1 - I_2 \quad (2)$$

Solving equations (1) & (2)

$$(1) I_1 + (0) I_2 = -3$$

$$(-1) I_1 + (5) I_2 = 0$$

$$I_1 = -3A$$

$$I_x = -I_1 = 3A$$

$$I_2 = -0.6A$$

$$V_x = 1(I_1 - I_2) = 1(-3 - (-0.6)) = -2.4V$$

